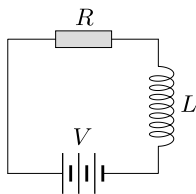


## T2: Thermal oscillations (10 pts)

A resistor is made of a material which undergoes a phase transition so that its resistance takes one of the two values,  $R_1$  if its temperature is smaller than  $T_c$ , and  $R_2 > R_1$  if the temperature is larger than  $T_c$ .



This resistor is connected to a voltage source through an inductor of inductance  $L$ . It appears that if the applied voltage  $V$  is between two critical values,  $V_1 < V < V_2$ , the temperature of the resistor starts oscillating. Assume that (i) the heat flux  $P$  from the resistor to the ambient medium is given by  $P = \alpha(T - T_0)$ , where  $\alpha$  is a constant,  $T$  denotes the temperature of the resistor, and  $T_0$  is the ambient temperature; (ii) the geometrical size of the resistor is so small that it will reach a thermal equilibrium much faster than the characteristic time  $L/R_2$ .

- (a) (2 pts) Express  $V_1$  and  $V_2$  in terms of the other parameters defined above.
- (b) (6 pts) Assuming that  $V_1 < V < V_2$ , sketch qualitatively how the temperature of the resistor  $T$  depends on time  $t$ , and find the ratio  $(T_{\max} - T_0)/(T_{\min} - T_0)$ , where  $T_{\max}$  and  $T_{\min}$  denote the maximal and minimal values of  $T$ , respectively.
- (c) (2 pts) Find the period of oscillations if  $V = \sqrt{V_1 V_2}$  and  $R_2 = 16R_1$ .