Problem 10. Black box ***(8 points)***

Determine the electric circuit inside the black box. It is known that apart from the wires and two resistors, the electric circuit includes four components. Equipment: black box with four output leads, a piece of wire.